

DIGITAL SYSTEMS AND MICROPROCESSORS (ELE2002M)

LECTURE 2 - GATE LEVEL MINIMIZATION

Instructor:

Assoc. Prof. Dr. Edmond Nurellari

Gate Level Minimisation

- Covered earlier
 - ▣ Sum of products
 - ▣ Boolean algebra
- This Lecture
 - ▣ Karnaugh maps
 - ▣ Some more examples of algebra and truth tables=

Karnaugh Maps

- K-Maps are a convenient way to simplify Boolean Expressions.
- They can be used for up to 4 or 5 variables.
- They are a visual representation of a truth table.
- Expression are most commonly expressed in sum of products form.

K-map revision

Simplify the Boolean Expression:

$$F(w,x,y,z) = \sum (1,3,7,11,15)$$

Which has don't care conditions

$$D(w,x,y,z) = \sum (0,2,5)$$

Solution

K-map revision

$$F(w,x,y,z) = \sum (1,3,10) + \sum_d (0,2,8,12)$$

Simplified expression for $F = ?$

Solution

De Morgan again

- A NAND gate:

$$Y = \overline{A.B} = \overline{A} + \overline{B}$$





is the same as an OR gate with two NOT gates

- Similarly a NOR gate is the same as an AND gate with two inverters

$$Y = \overline{\overline{A} + \overline{B}} = \overline{\overline{A}}.\overline{\overline{B}}$$

- not the individual terms
- change the sign
- not the lot

Dual gates

    

- **NOT** the individual inputs
- **Change the gate**
- **NOT** the output

Truth Tables and Boolean Notation


NAND Gate Representation

- It is possible to implement any Boolean expression using only NAND gates




Two Graphic Symbols for NAND

NOT

 


AND

 



OR
 
$$A + B = \overline{\overline{A} \cdot \overline{B}}$$



Two Level Implementation using NAND


$$F = AB + CD$$

  

Truth Tables and Boolean Notation


□ NAND Gate representation

 ▣ Implement the following circuit using only NAND gates






Solution

 - Dual the gates, remember two NOTs together can be removed.



AND feeding OR

   

Example

Implement the following Boolean function using NAND gates

$$F(x,y,z) = \sum (1,2,3,4,5,7)$$

First reduce using K-map

F =

Multi-level NAND Gates

General Procedure for converting a multi-level AND-OR diagram into all-NAND diagram:

1. Convert all AND gates to NAND gates with AND-Invert symbol
2. Convert all OR gates to NAND gates with invert-OR symbol
3. Check all bubbles in the diagram. For each bubble that is not compensated by another circle along same line, insert an inverter (a one-input NAND gate) or complement the input literal.

Multi Level NAND Example

$$F = (AB' + A'B)(C+D)$$


Solution

NOR Gates


- Implement NOT, AND and OR using NOR gates

- Example

AND gate






 


dual circuit:

 

Solution

      - Similar pattern to using NAND gates (not surprising)



Homework Exercise

- NOR Gate representation
 - ▣ It is also possible to implement any Boolean expression using only NOR gates
 - ▣ Implement the following circuit using only NOR gates

